


BRASSM (Maestro Brass Master Replica) Stage 3 Wiring

Version 2017November13

Copyright 2009, 2017 JD Sleep

Permission refused for posting/serving this file from any site other than www.generalguitargadgets.com

Trademarks are property of their owners

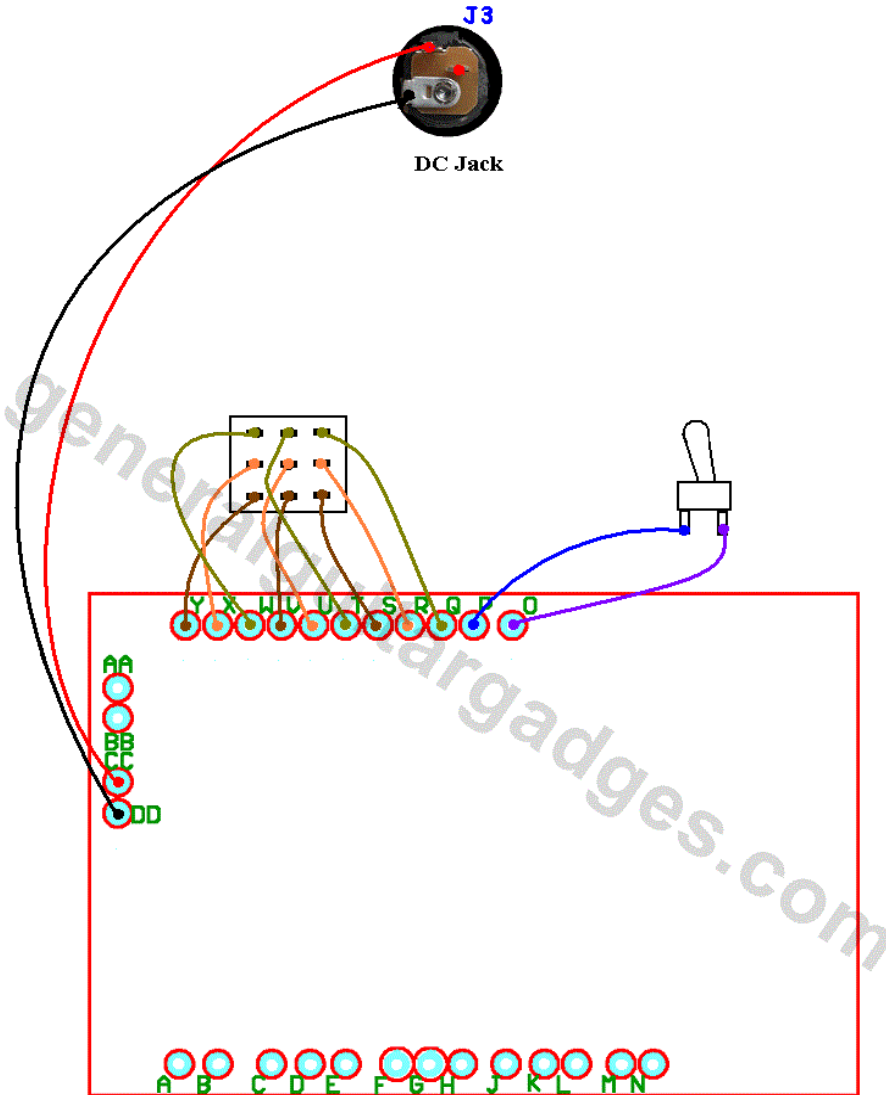

Stage 3 wiring: Wire the Toggle switches from the pads on the upper side of the PCB. Wire the 9v power and ground (pads “CC” and “DD”) from the PCB to the DC Jack.