

## IC Buffer A/B Input/Buffered Output on an ABY Switch

Version 2014January27

Copyright 2014 JD Sleep

Permission refused for posting/serving this file from any site other than www.generalguitargadgets.com

Trademarks are property of their owners

Here's an A/B/Y implementation for A/B/Y'ed inputs into a single buffered output. This might be useful for two instruments going into the same rig.

