



FolkUrban Music LofMoFo Project

Version 2014JULY29

Copyright 2014 JD Sleep

Permission refused for posting/serving this file from any site other than www.genealguitargadgets.com

Thanks to Tim Escobedo for this Project.

This will give you a lo-fi sound as if your guitar is coming out of a cheap transistor radio.

Bill of Materials

Resistors (1/4 watt rating)

3 – 100k

Pots (1/4 watt or higher rating)

1 – 500k linear

1 – 100k log

Transistors

1 – 2N2222 or other low gain, low quality transistor.

Capacitors (minimum 16 volt rating)

1 – 220pF ceramic

2 – 0.01uF film

2 – 0.1uF film

Other

1 – 1N5817 diode

1 – 3PDT or DPDT heavy duty foot switch (bypass)

1 – mono quarter inch jack

1 – stereo quarter inch jack


9v battery snaps & holder and/or DC jack,

knobs, Copper-clad board, etchant, or

perfboard

24 gauge stranded wire

Enclosure

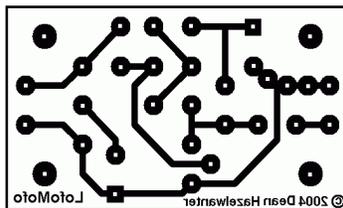

Size 4.6cm x 2.7cm

FolkUrban Music LofMoFo Project

Version 2014JULY29

Copyright 2014 JD Sleep

Permission refused for posting/serving this file from any site other than www.generalguitargadgets.com

