


Typical Stompbox DC Jack and Battery Wiring Diagram

Version 2012January17

Copyright 2012 JD Sleep

Permission refused for posting/serving this file from any site other than www.guitar-gadgets.com

Trademarks are property of their owners

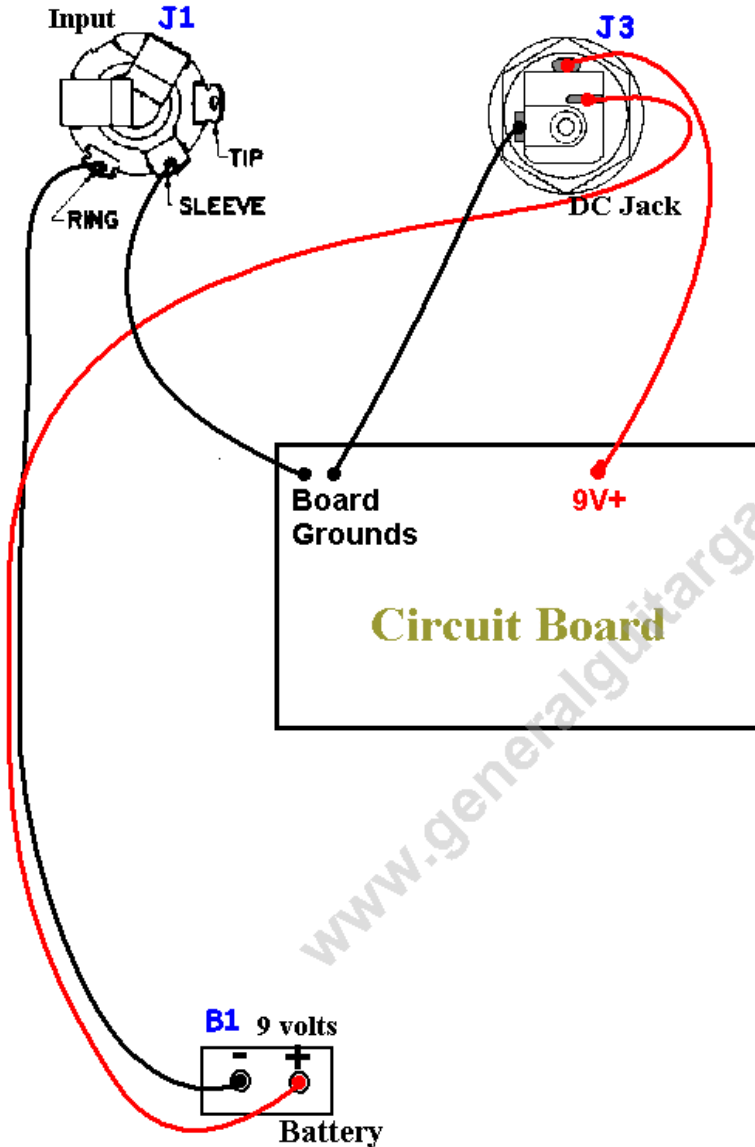

Typical stompbox connections for options of DC Jack or Battery power. J3 shows the back side of a coax DC Jack with a normally closed switch on the 3rd lug where the positive lead of the battery is connected. When the DC Jack is plugged in, the battery connection is disconnected.