

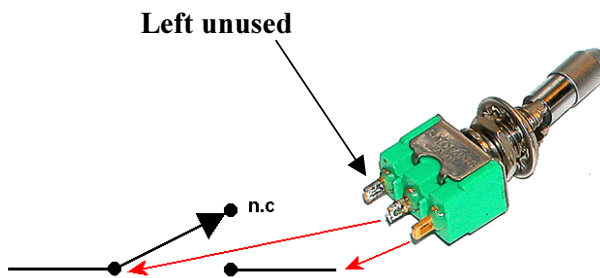


## Switches

### SPDT

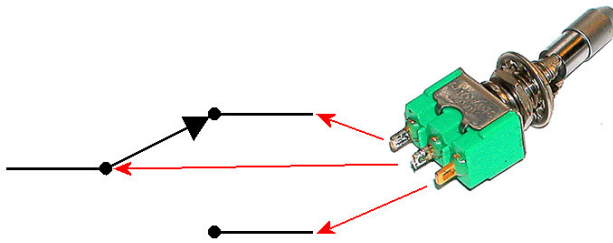


### DPDT

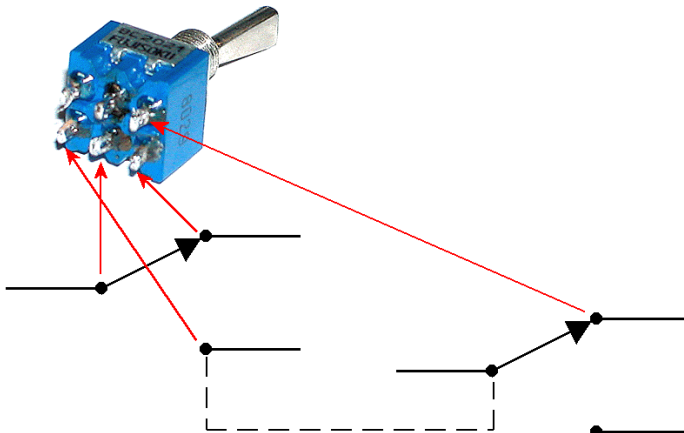

**Two switches in one package (unit).**

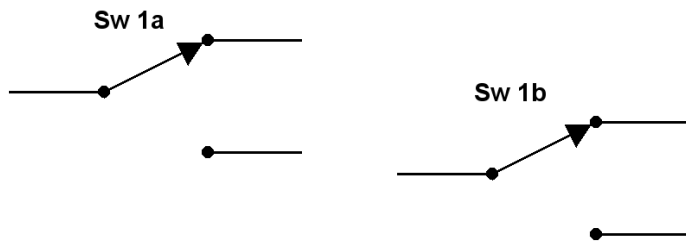
**The second switch connects in the same way to the three lugs above, make sure to connect the arrow points in the same side at the switch.**

Sometimes also looks like this in schematics.


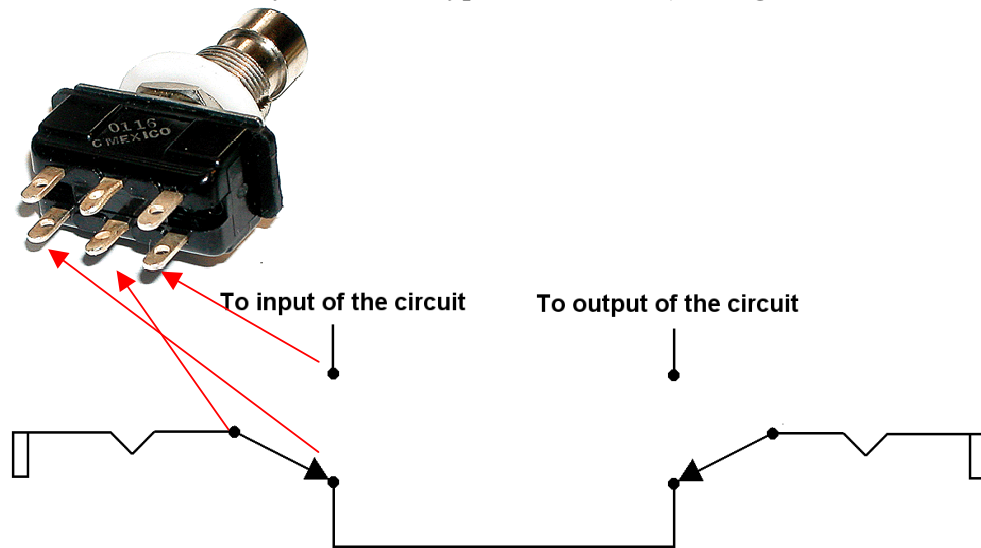
### DPDT stompswitch

Most of the times they're used to bypass the effects (turning the effect in or out).



The second switch connects as the first one  
Often the true by pass drawing is not shown in schematics, just add it if you need it.

This is how it looks reality

